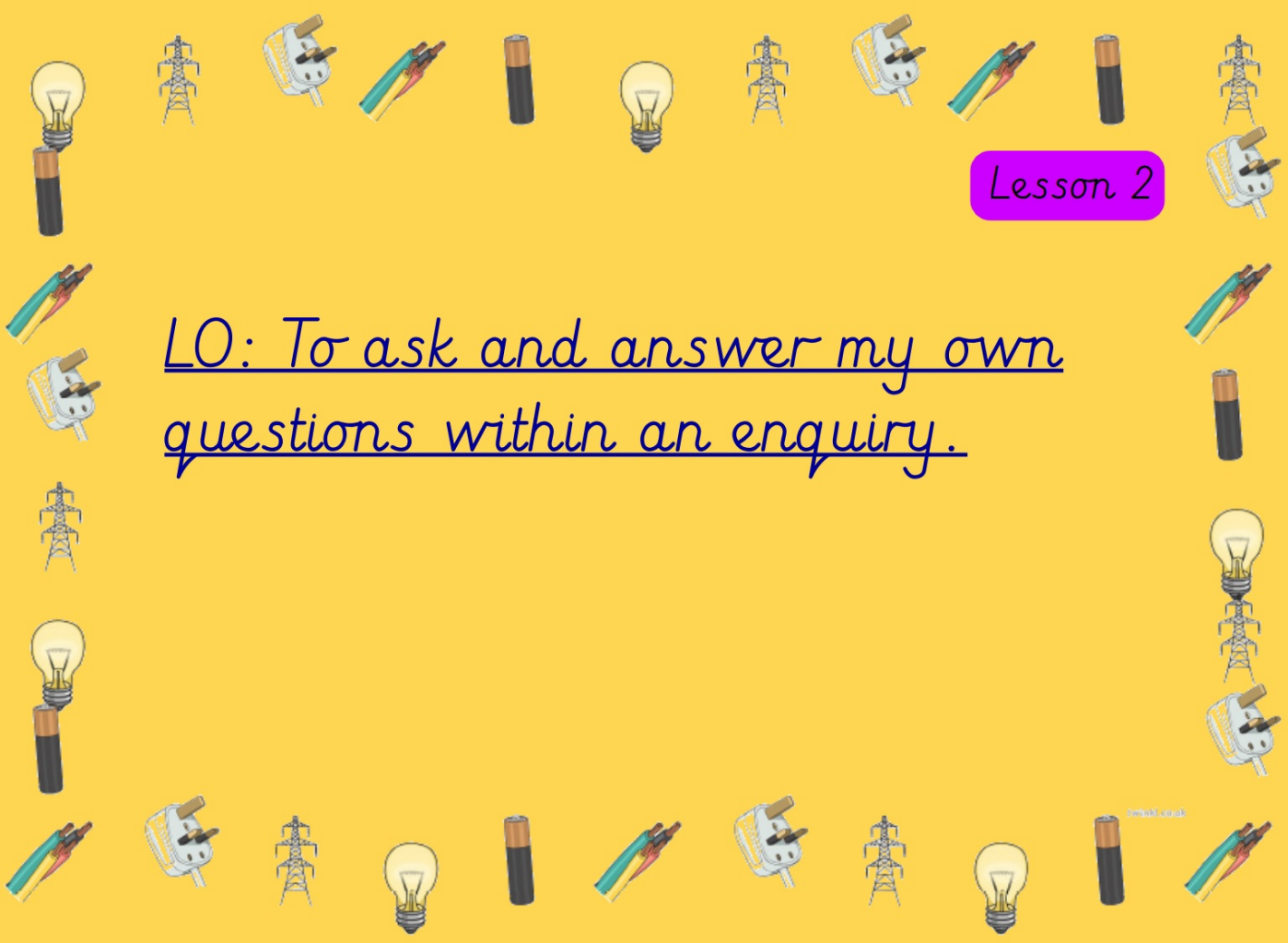


Lesson 2

LO: To ask and answer my own questions within an enquiry.




squishy circuits




closed loop

one-way system

short circuit

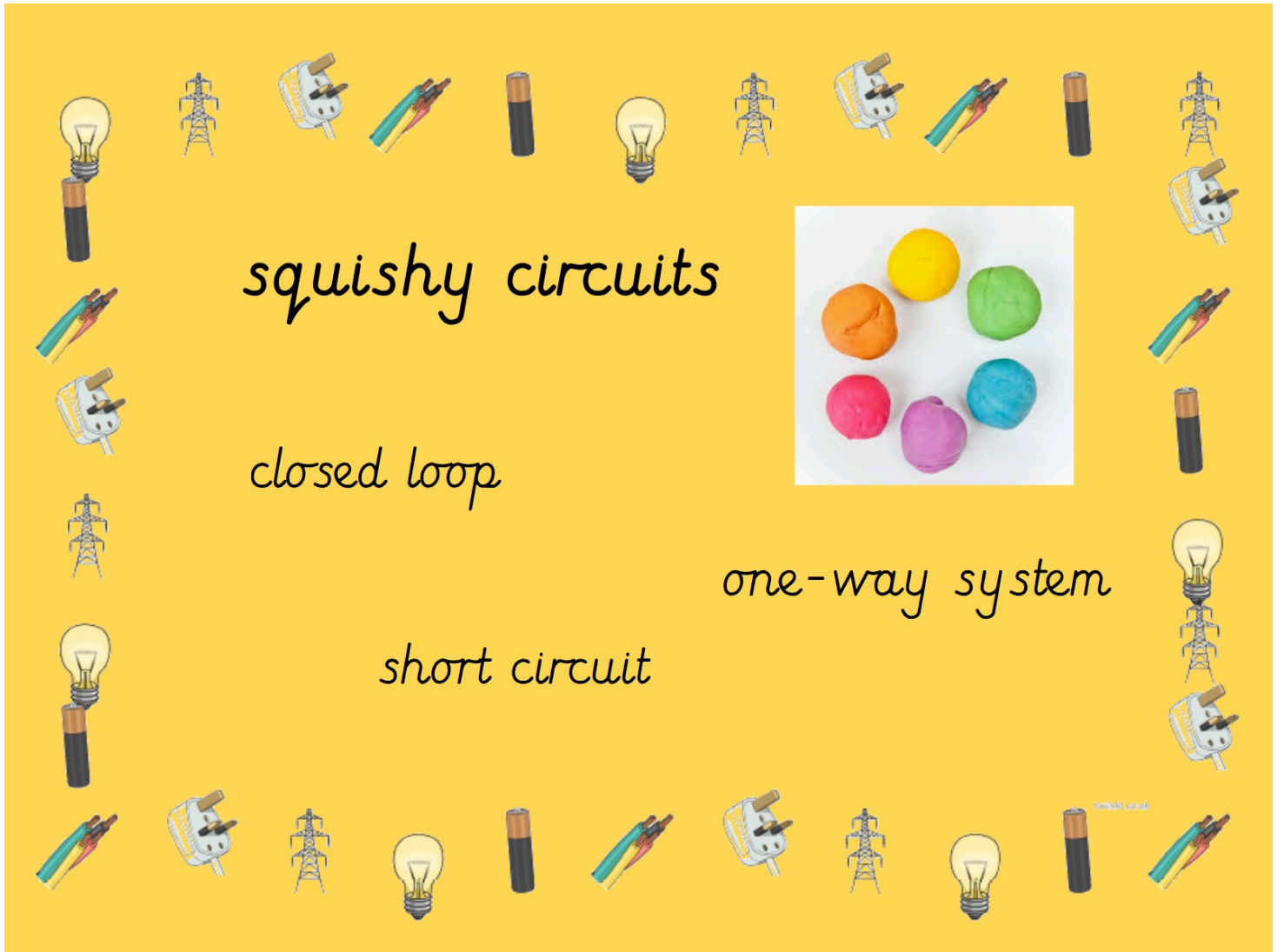

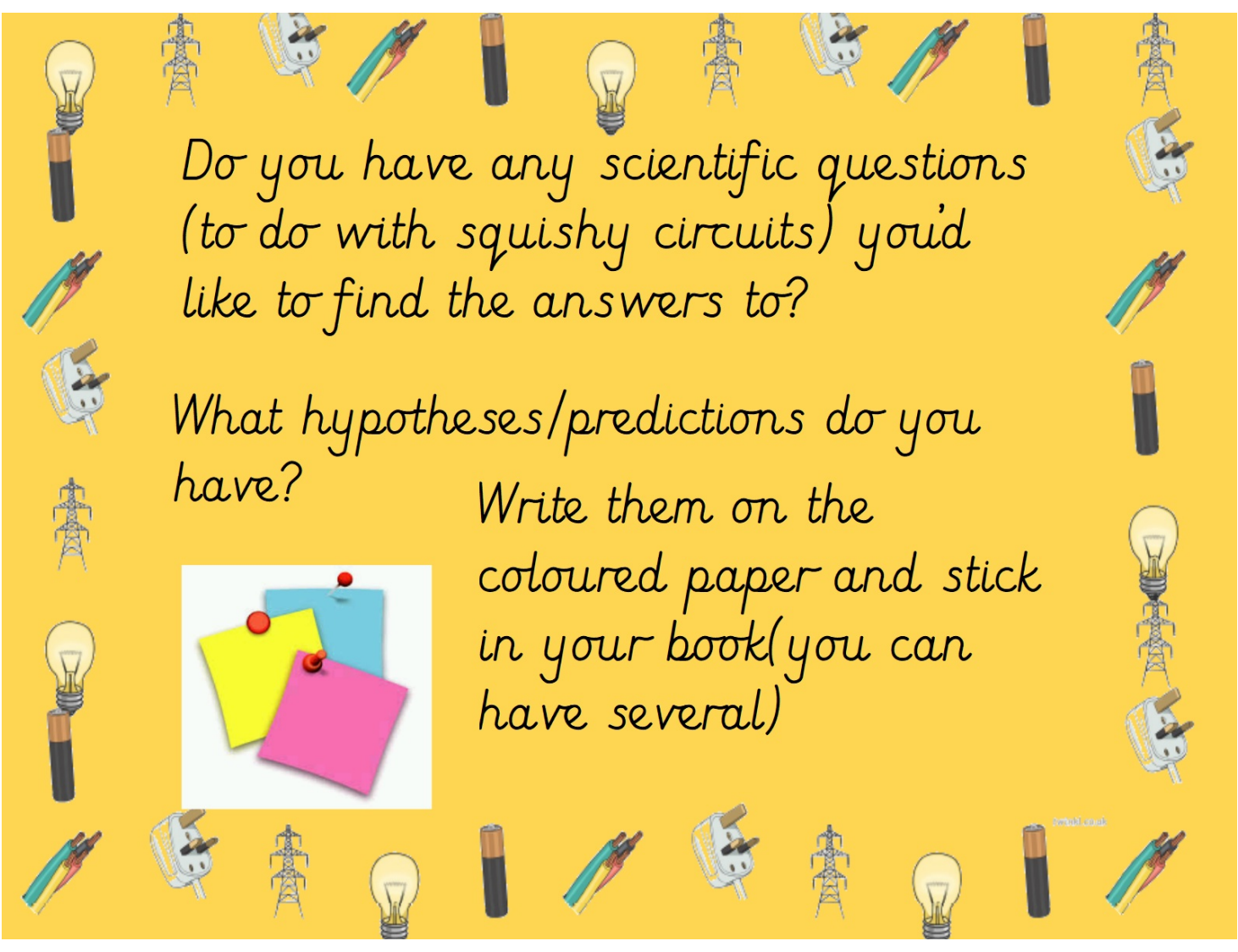


Do you have any scientific questions
(to do with squishy circuits) you'd
like to find the answers to?

What hypotheses/predictions do you
have?



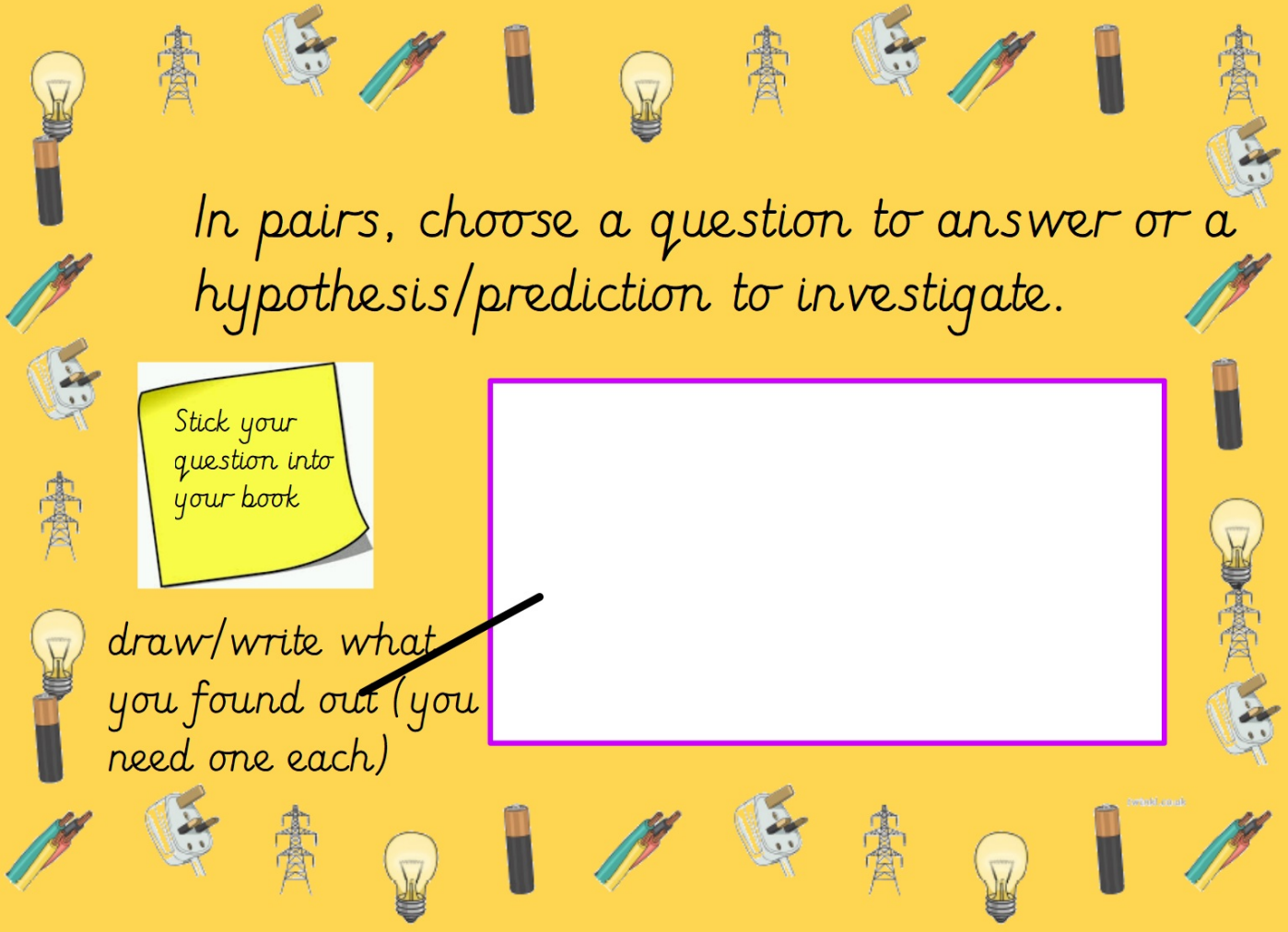Write them on the
coloured paper and stick
in your book (you can
have several)



In pairs, choose a question to answer or a hypothesis/prediction to investigate.

Stick your question into your book

draw/write what you found out (you need one each)

